

## Lecture 10

# Reference Design Inverter Schematics: Microcontroller & Communication Circuits

### Objectives:

- Discuss Analog-to-Digital (A2D) conversion, the sample-and-hold process, and a basic R-2R Digital-to-Analog (D2A) circuit for obtaining a digital value.
- Discuss Nyquist-Shannon Sampling Theorem and the concept of aliasing.
- Examine RC filter values, cut-off frequencies, and phase distortion of sampled control signals.
- Discuss other peripheral circuits for the digital signal processor (DSP), such as the external EEPROM, communication circuits, and step-down supply.
- Discuss debugging circuits for monitoring digital or analog DSP signals.

### Keywords:

Analog-to-Digital (A2D) conversion

Digital-to-Analog (D2A) conversion

R-2R Resistive Ladder circuit

Nyquist-Shannon Sampling Theorem

Signal Aliasing

RC filter response

External EEPROM

RS-232 serial communication

JTAG & ICSP programming ports

Digital Signal Processor (DSP)

Inter-Integrated Circuit (I2C) bus

Serial Peripheral Interface (SPI) bus

## Overview of Inverter Control Schematics

Discuss the different sections of the schematic

# EE-499 Three-Phase AC Motor Control

